



A 4-to-1 multiplexer diagram. The inputs are labeled 0, 1, 2, and 3. The outputs are labeled mem, +4, null, and jump[1].